



INSTRUCTION cum EXPERIMENTS MANUAL

Analogue Digital Trainer

Model SCI-DTK 01E

TABLE OF CONTENTS

Sr No.	Description	Page No.
1	Warranty certificate	3
2	System Specifications	4
3	Block Diagram	6
4	Hardware Description	7
5	Introduction	7
6	Hardware Installation	12
7	Experiments	13
8	Experiment 1: Study of operation of all Logic Gates	14
9	Experiment 2: Study of Binary Adders	16
10	Experiment 3: Study of Binary Subtractors	19
11	Experiment 4: Study of Binary to Gray Code Conversion	20
12	Experiment 5: Study of Binary to Gray Code Conversion	22
13	Experiment 6: Study of Gray Code to Binary Code Conversions	26
14	Experiment 7: Study of Characteristics of various types of Flip-Flops	28
15	Experiment 8: Study of Crystal Oscillator	29
16	Experiment 9: Study of 4 bit Binary up down Counter	30
17	Experiment 10: Study of Johnson Counter	31
18	Experiment 11: Study of 4 Bit Serial in Parallel out Shift Register	33
19	Experiment 12: Study of 10 to 3 Line Encoder	34
20	Experiment 13: Study of 3 to 10 Line Decoder	35
21	Experiment 14: Study of Multiplexer and De-multiplexer Circuit	37
22	Experiment 15: Study of Pulse Stretcher Circuit	39
23	Experiment 16: Study of method of Interfacing CMOS Logic family with TTL family	40
24	PIN DIAGRAMS OF ICs	41

WARRANTY CERTIFICATE

Supply of **Sci-tech Analogue Digital Trainer Model SCI-DTK 01E**

The above instrument is warranted to be free from defects in workmanship and material and if it proves so defective within 15 (Fifteen months) calendar months from the date of shipment to the original purchaser, named above it shall be repaired or replaced free of charge provided

**The Purchaser sends promptly to: M/s. SCI-TECH UK LIMITED
Kemp House, 160 City Road, London EC1V 2NX, UNITED KINGDOM**

Tel: ++ 44 2081238067.

Website: www.scitechdidactic.com

E-mail: internationalsales@scitechdidactic.com,

notice of defect and satisfactory proof thereof as assuring that the instrument/equipment has been properly maintained and operated within the limits of rated capacity and normal usages, and

- Assumes the obligation of all expenses of returning the defective instrument, properly packed to the Factory at the address given in (a) above, if required.
- On parts of products incorporated in the instrument but not manufactured by M/s. **SCI-TECH UK LIMITED**, this warranty is limited to extending to the purchaser the same warranty as given by the supplier of such part or products.

This guarantee does not cover consumable parts such as Bulbs, Fuses, and Rubber Seals etc.

Under the circumstances shall M/s **SCI-TECH UK LIMITED**, have any liability whatsoever for loss of use or for any indirect or consequential damages.

We can only undertake to send our men to a distance to investigate and put right alleged defects on the distinct understanding that we are paid for their time and expenses in every case.

M/s. **SCI-TECH UK LIMITED** decision about repairing or replacing the equipment or its parts will be final and binding on all concerned parties.

Unless superseded or in contractual form, this warranty is made expressly in lieu of all the other liabilities and obligations on our part.

For **SCI-TECH UK LIMITED**

Place: London/United Kingdoms.


SPECIFICATIONS

- **Indicators**
 - 16 TTL/CMOS Logic Level Inputs with Dual Color LED indication for logic low and logic high
 - 16 LED for output indication
- **Clock Generator**
 - Fixed Clock generation of 1Hz, 10Hz, 100Hz, 1KHz, 100KHz & 1MHz
- **Pulse Generator**
 - Two Pulser Generators provides four de-bounced Outputs
 - Logic Pulsar provides single pole double throw bounce less pulses of Low to High and High to Low transitions
- **Logic Probe**
 - Logic Probe facility provided with LED indicators to indicate Logic High & Low
- **On Board Applications**
 - Variable potentiometers of 1K & 1M provided on board
 - DPMs (4 no) with mode selection: DC volt/ current.
 - Buzzer for alarm application with termination on 2mm banana Socket
 - +12V SPDT Relay for Control application with termination on 2mm banana Socket
 - Two numbers of BNC Connectors with termination on 2mm banana Socket for CRO applications
- **Bread Board Area**
 - Four Distribution Strip of 100 tie points each totaling 400 tie points
 - Two Terminal Strip of 630 tie points totaling 1260 tie points
- **Function Generator**
 - Provides Sine, Square (TTL) and Triangular output waveforms.
 - Frequency variable from 0- 200KHz in Five steps.
 - Sine/Traingle Output Voltage is 20V p-p max.
- **Display**
 - Two numbers of seven-segment LED display
 - Two numbers of Hex to seven-segment LED display
 - LED BAR graph with 10 LED indicators to display 0-5 V input
 - Input terminations of Displays on 2mm Banana sockets
- **Power Supplies**
 - Fixed DC Power Supply: +5V/2A, $\pm 12\text{V}/250\text{mA}$.
 - Variable DC Power supply 0 to +15V/250mA, 0 to -15V/250mA & 0 to +30V/250mA.
 - AC Power Supply of 15V-0-15V
- **Interconnections**
 - All interconnections are made using 2mm banana Patch cords.
 - Set of 2mm Patch cords for interconnections
- All ICS are mounted on IC Sockets.
- Supports KMS series ready to use Electronics board
- Bare board Tested Glass Epoxy SMOBC PCB is used.
- Attractive Metallic enclosures.

- User's Manual

A large, faded version of the sci-tech logo, consisting of a green and purple swoosh and the text "sci-tech" in a large, grey, sans-serif font.


BLOCK DIAGRAM

 

HARDWARE DESCRIPTION



Fixed Clock (Block-12)

Sci-tech Analogue Digital Trainer Model SCI-DTK 01E uses a IC 74LS04 analog with a 4.00MHz crystal to generate a clock of 4MHz which is then divided by IC 74LS93 to achieve 1MHz clock frequency. The Clock level is made compatible with TTL and CMOS levels. This clock is then divided using ICs CD4518 and CD4013B to generate the frequencies of 1Hz, 10Hz, 100Hz, 1 KHz, 100 KHz & 1 MHz are brought out at six 2mm terminals through no inverting buffers.

 


Manual Clock (Block-9)

  The system uses a CMOS NAND GATE IC CD4011 to generate a manual clock whenever a push button switch is pressed and released. The pressing of the button changes the Q and /Q outputs of the Flip- Flop and so positive going pulse and negative going pulse are generated. These can be tapped from 2mm terminals marked as High to Low Transition & Low to High Transition on the Digital Trainer Board.




Logic Probe (Block-14)

The system use CMOS inverter IC CD4049 to sense logic LOW and logic HIGH. On reserving a pulse input both LED glow one by one but if the frequency is high then these two LEDs RED and GREEN appear to be glowing continuously. The logic probe can be used by inserting a probe lead in the 2mm terminal marked as logic input. The other end of the probe touched to a logic HIGH, the Red LED glows OR the probe is touched to logic LOW the Green LED glows. If the probe is touched to a pulse signal, the Red and Green LEDs flash if the frequency is low else both will appear to be glowing continuously.

 


Seven Segment Display (Block-13)

 Sci-tech Analogue Digital Trainer Model SCI-DTK 01E provides Two Seven Segment, Two Hex to Seven Segment displays and one BAR Graph Display on the board so that experiments involving displays can be conducted. The four seven segment display can be used as individual segment control. All the inputs are terminated on 2mm Banana Sockets for user applications




TTL/CMOS Logic Levels Input (Block-4)

The Digital Trainer has 16 Push Key Switch S1 to S16 to generate ten TTL/CMOS input named as I1 to I16 as marked on the Trainer Board. When the Switch is in Normal Mode, Logic Level High will generate & when the switch is in Push Mode, Logic Level Low will be generated on the 2mm banana socket provided on the kit. 16 Dual Color LEDs are used to indicate the logic input generated by each Push Key switch. The logic HIGH is indicated by the corresponding LED glowing as RED where the Logic LOW is indicated by the LED glowing as GREEN.

 


Logic Level Output Indicator (Block-1)

 This Trainer has 16 Logic Level LED indicators for indicating output. The Logic high is indicated by LED glowing, where the logic low is indicated by LED is not glowing. Logic level output is given in 2mm banana socket provided on-board.



Function Generator (Block-2)

 Onboard 200 KHz Function Generator generating Sine, Square & Triangle signals. Selector Switch is provided for five different frequency range selection of 20Hz, 200Hz, 2 KHz, 20KHz & 200KHz. The Frequency of Sine, Square & Triangle can vary from the Frequency adjust pot. The Amplitude of sine & triangle can vary by Amplitude adjust pot. The Amplitude of Square wave output is fixed.




Bread Board Area (Block-5)

This Trainer provides a bread board area consisting of two Terminal Strip of 630 Tie points each totaling 1260 Tie points and Four Distribution Strip of 100 Tie points each totaling 400 Tie points




Variable Potentiometer (Block-3)

 This Trainer provides on-board Variable Pot for 1K & 1M for any digital/analog experiments.




Fixed DC Supply (Block-6, 7, 8)

 This Trainer provides on-board Fixed DC Power Supply of +5V/ 1A, GND, +12V/250mA, -12V/250mA. These Power terminals are provided in 2mm Banana Socket.




Variable DC Supply (Block-11)

 This Trainer has provision for on-board three different Variable DC Power Supplies. They are from 0 to +15V/250mA, 0 to -15V/250mA & 0 to 30V/250mA. These Output Power terminals are provided in 2mm Banana Socket. For varying the voltage POT is provided on-board.




AC Supply (Block-10)

 This Trainer provides on-board AC Power Supply of 15V-0-15V. These Power terminals are provided in 2mm Banana Socket.




RELAY (Block-00)

 This Trainer provides on-board Relay circuit. These Power Coil and Output terminals are provided in 2mm Banana Socket for user applications.




BUZZER (Block-00)

 This Trainer provides on-board Buzzer circuit. The Input to buzzer is provided using 2mm Banana Socket for user applications.




BNC Termination (Block-00)

 This Trainer provides on-board circuit for BNC Termination. BNC Termination for CRO application is provided on board. The Input to BNC connector is provided using 2mm Banana Socket.



Digital Panel Meter (Block-00)

This Trainer provides on-board four circuits for Digital Panel Meter (DPM). Two of these are Voltmeters with range selection between 2V and 200V and rest two are Ammeters with range selection between 200mA and 2mA. The Input to DPMs is provided using 2mm Banana Socket and are provided through corresponding V(+) and V(-) or A(+) and A(-) Terminals.. Each Panel meter is provided with a switch for range selection.

 

INTRODUCTION

Sci-tech Analogue Digital Trainer Model SCI-DTK 01E has been designed with the idea of providing basic facilities essential for conducting simple experiments in the laboratory. Using these facilities one can get oneself familiarized with the various digital ICs. The system is suitable for conducting experiments on TTL as well as CMOS ICs.

INSTALLATION

Sci-tech Analogue Digital Trainer Model SCI-DTK 01E works on 230V, 50Hz power supply. By connecting 230V power point is by means of the power code of the Trainer. Please follow the below instruction while installing the Trainer.

1. Connect the Trainer kit to 230V power point.
2. Switch ON the power supply provided in the rear end of the kit.
3. Now your kit is ready for conducting the experiments on different ICs.

Note: Please take precaution to turn OFF the power supply while connecting the circuits.

A large, faded version of the sci-tech logo is centered on the page, serving as a background watermark. It features the same stylized 's' and 'sci-tech' text as the header logo.

sci-tech

EXPERIMENTS







EXPERIMENT 1

Objective: Study of operation of all Logic Gates

Components Needed:

S.N	Components	Quantity
1.	IC 7408 2 input AND Gate.	1
2.	IC 7432 2 input OR Gate.	1
3.	IC 7400 2 input NAND Gate.	1
4.	IC 7402 2 input NOR Gate	1
5.	IC 7486 2 input EX-OR Gate	1
6.	IC 7404 NOT Gate.	1

Logic diagrams and IC Pin diagrams:

      

Truth Tables:

Input 1	Input 2	Output
X	Y	O
0	0	0
0	1	0
1	0	0
1	1	1

AND Gate

Input 1	Input 2	Output
X	Y	O
0	0	1
0	1	1
1	0	1
1	1	0

NAND Gate

Input 1	Input 2	Output
X	Y	O
0	0	0
0	1	1
1	0	1
1	1	1

OR Gate

Input 1	Input 2	Output
X	Y	O
0	0	1
0	1	0
1	0	0
1	1	0

NOR Gate

Input 1	Input 2	Output
X	Y	O
0	0	0
0	1	1

Input	Output
0	1
1	0

1	0	1
1	1	0

EX-OR Gate

NOT Gate

Procedure:

AND Gate:

1. Connect +5 V to pin no. 14 of IC 7408 and connect ground to pin no.7(refer IC pin diagram)
2. Apply 0 (0 V) to pin no. 1 and 2 of IC 7408 shown in figure as per Truth Table.
3. Connect output of AND Gate i.e pin no.3 to input of logic probe or 10 bits LED display.
4. Switch on the instrument.
5. Observe output of Gate on 10 bits LED display.
6. Outputs can also be observed on oscilloscope.
7. Repeat steps 2, 3, 4 for different input combination.
8. Verify Truth Table.

NAND Gate:

1. Connect +5 V to pin no. 14 of IC 7400 and ground to pin no. 7.(Refer IC pin diagram)
2. Apply 0 (0 V) to pin no. 1 & 2 of IC 7400 shown in figure as per Truth Table.
3. Connect output of NAND Gate i.e. pin no.3 to input of logic probe or 10 bits LED display.
4. Switch on the instrument.
5. Observe output.
6. Repeat Step 2, 3, 4 for different input combinations.

OR Gate:

1. Connect +5 V to pin no. 14 of IC 7432 and connect ground to pin no.7 (Refer IC pin diagram)
2. Apply 0 (0V) to pin no. 1 and 2 of IC 7432 shown in figure as per Truth Table.
3. Connect output of OR Gate i.e pin no. 3 to input of logic probe or 10 bits LED display.
4. Repeat step 4, 5, 6 of NAND Gate.

NOR Gate:

1. Connect + 5V to pin no. 14 of IC 7402 and connect ground to pin no.7
2. Apply 0 (0V) to pin no. 2 and 3 of IC 7402 as per Truth Table.
3. Connect output of NOR Gate i.e. pin no. 1 to input of logic probe or 10 bits LED display.
4. Repeat step 4, 5, 6 of NAND Gate.

EX-OR Gate:

1. Connect +5V to pin no. 14 of IC 7486 and connect ground to pin no.7
2. Apply 0 (0V) to pin no. 1 and 2 of IC 7486 as per Truth Table.
3. Connect output of EX-OR Gate i.e pin no. 3 to input of logic probe or 10 bits LED display.
4. Repeat step 4, 5, 6 of NAND Gate.

NOT Gate:

1. Connect +5 V to pin 14 and ground to pin no.7 of IC 7404.
2. 0 (0V) to pin no. 1 of IC 7404 as per Truth Table.
3. Observe output on 10 bits LED display or Logic Probes

EXPERIMENT 2

Objective: Study of binary adders

- A. Half Adder
- B. Full Adder
- C. Two Bit Binary Parallel Adder

A. Half Adder

Components Needed:

S.N	Components	Quantity
1.	IC 7408 2 input AND Gate.	1
2.	IC 7486 2 input EX-OR Gate.	1

Logic diagram:

 


Figure 2

Truth Table :

Input1	Input2	Carry	Sum
X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Procedure:

1. Make connections as shown in figure.
2. Connect +5V to pin no. 14 and ground to pin no.7 of IC 7408 and IC 7486. See IC Pin diagram.
3. Connect 0 (0V) to input x and y of adder shown as per Truth Table.
4. Switch ON the instrument.
5. Observe outputs S and C on 10 bits LED display.
6. Outputs can also be observed on oscilloscope.
7. Repeat steps 4,5,6,7 for other input combinations.
8. Verify Truth Table.

B. Full Adder:

Component s Needed:

S.N	Components	Quantity
1.	IC 7408 2 input AND Gate	1
2.	IC 7432 2 input OR Gate	1
3.	IC 7486 2 input EX-OR Gate	1

Logic diagram:

 


Figure 3

Truth Table:

Input 1	Input 2	Input Carry	Output Carry	Sum
X	Y	Ci	Co	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


Procedure: Same as above

C. Two Bit Binary Parallel Adder

Component s Needed:

S.N	Components	Quantity
1.	IC 7400 2 input NAND Gate	1
2.	IC 7486 2 input EX -OR Gate	1
3.	IC 7404 Not Gate	1

Logic diagram:

 

Truth Table:

Sr. No.	Input 1 Bit 1	Input 2 Bit 2	Input 1 Bit 1	Input 2 Bit 2	Carry	Sum	Sum
	A1	A0	B1	B0	C0	S1	S0
1	0	0	0	1	0	0	1
2	0	1	0	1	0	1	0
3	0	1	1	1	1	0	0
4	1	0	1	0	1	0	0
5	1	0	1	1	1	0	1

Procedure:

1. Make connections as shown in figure.
2. Connect +5V to pin no. 14 and ground to pin no.7 of ICs.
3. See IC Pin diagram.
4. Connect 0 (0V) and 1 (+5 V) to inputs A1, A0, B1, B0 of adder shown as per truth table
5. Switch ON the instrument.
6. Observe outputs S1, S0 and C0 on 10 bits LED display.
7. Outputs can also be observed on oscilloscope.
8. Repeat steps 4, 6 for other input combinations.
9. Verify Truth Table.

Observation and Result:

Full adder can be implemented using two half Adder. Adders are studied and Truth Tables are verified.

EXPERIMENT 3

Objective: Study of Two Bit Binary Subtractor (Half Subtractor)

Components Needed:

S.N	Components	Quantity
1.	IC 7486 2 input EX-OR Gate.	1
2.	IC 7408 2 input AND Gate	1
3.	IC 7404 NOT Gate.	1

Logic diagram:

 


Figure 5

Truth Table:

Input 1	Input 2	Borrow	Difference
X	Y	B	D
0	0	0	0
0	1	1	1
1	0	0	1
1	1	0	0

Procedure:

1. Make connections as shown in figure.
2. Connect +5 V to pin no. 14 and ground to pin no.7 of ICs.
3. See Pin diagram.
4. Apply 0 (0V) to input x and y of subtractor shown as per Truth Table.
5. Switch ON the instrument
6. Observe outputs **B** and **D** on 10 bits LED display.
7. Outputs can also be observed on oscilloscope.
8. Repeat steps 4, 6, and 7 for other input combinations.
9. Verify Truth Table.

EXPERIMENT 4

Objective: Study of Binary to Gray Code Conversion

Components Needed:

S.N	Components	Quantity
1.	IC 7486 2 input EX-OR Gate	2
2.	IC 7404 NOT Gate	1

Logic diagram:

 


Figure 6

Truth Table:

Binary Code				Gray Code			
B3	B2	B1	B0	G3	G2	G1	G0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	0
0	1	0	1	0	1	1	1
0	1	1	0	0	1	0	1
0	1	1	1	0	1	0	0
1	0	0	0	1	1	0	0
1	0	0	1	1	1	0	1
1	0	1	0	1	1	1	1
1	0	1	1	1	1	1	0
1	1	0	0	1	0	1	0
1	1	0	1	1	0	1	1
1	1	1	0	1	0	0	1
1	1	1	1	1	0	0	0

Procedure:

1. Make connections as shown in figure.
2. Connect +5V to pin no. 14 and ground to pin no.7 of ICs.
3. See Pin diagram.
4. Apply 0 (0V) to binary inputs B3, B2, B1, B0 shown as per Truth Table.
5. Switch ON the instrument
6. Observe outputs G3, G2, G1, G0 on 10 bits LED display.
7. Outputs can also be observed on oscilloscope.
8. Repeat steps 4, 6, 7 for other input combinations.
9. Verify Truth Table.

Result and Observation:

Binary to gray code conversion is studied. Most significant bit of binary as well as gray code is same as far as 4 bit code is concerned.

A large, light gray watermark of the sci-tech logo and text is centered on the page, partially obscured by a large, stylized, multi-colored swoosh graphic.

EXPERIMENT 5

Objective: Study Gray Code to Binary Code Conversions

Components Needed:

S.N	Components	Quantity
1.	IC 7486 2 input EX-OR Gate	2

Logic Diagram:

 


Figure 7

Truth Table:

Gray Code				Binary Code			
G3	G2	G1	G0	B3	B2	B1	B0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	1	0	0	1	0
0	0	1	0	0	0	1	1
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	1
0	1	0	1	0	1	1	0
0	1	0	0	0	1	1	1
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	1
1	1	1	1	1	0	1	0
1	1	1	0	1	0	1	1
1	0	1	0	1	1	0	0
1	0	1	1	1	1	0	1
1	0	0	1	1	1	1	0
1	0	0	0	1	1	1	1

Procedure :

1. Make connection as shown in figure (Refer pin diagram of IC)
2. Connect +5 V to pin no. 14 and ground to pin no. 7 of IC 7486.
3. Apply Gray code inputs G0, G 1, G2, G3 as per Truth Table.
4. Switch ON the instrument.
5. Observe outputs on 10 bits LED display.
6. Repeat above step for other input combinations.
7. Verify Truth Table.

A large, light gray watermark of the sci-tech logo and text is centered on the page.

EXPERIMENT 6

Objective: Study of Binary to Excess -3 Code Conversion

Components Needed:

S.N	Components	Quantity
1.	IC 7432 2 input OR Gate.	1
2.	IC 7408 2 input AND Gate	1
3.	IC 7404 Not Gate	1

Logic diagram:

 


Figure 10

Procedure:

1. Make connection as shown in figure (Refer pin diagram of ICs)
2. Connect +5V to pin no. 14 and ground to pin no. 7 of ICs.
3. Connect 0 (0V) to binary inputs B3 B2 B1 B0 as per Truth Table.
4. Switch ON the instrument.
5. Observe outputs on 10 bits LED display.
6. Repeat steps 3, 5 for other input combinations.
7. Verify Truth Table.

Truth Table:

B3	B2	B1	B0	E3	E2	E1	E0
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0
1	0	1	0	1	1	0	1
1	0	1	1	1	1	1	0
1	1	0	0	1	1	1	1



EXPERIMENT 7

Objective: Study of Characteristics of various types of Flip-Flops

Components Needed:

S.N	Components	Quantity
1.	IC 7408 2 input AND Gate	2
2.	IC 7432 2 input OR Gate	1
3.	IC 7400 2 input NAND Gate	1
4.	IC 7402 2 input NOR Gate	1

Logic diagram:

 


Figure 9

Truth Table :

Clocked RS

Flip Flop JK flip flop

Present state	Input 1	Input 2	Next State	Present state	Input 1	Input 2	Next State
Q	S	R	Q(t+1)	Q	J	K	Q(t+1)
0	0	0	0	0	0	0	0
0	0	1	0	0	0	1	0
0	1	0	1	0	1	0	1
0	1	1	In determinant	0	1	1	1
1	0	0	1	1	0	0	1
1	0	1	0	1	0	1	0
1	1	0	1	1	1	0	1
1	1	1	In determinant	1	1	1	0

Present state	Input	Next state
Q	T	Q (t+ 1)
0	0	0
0	1	1
1	0	1
1	1	0

T Flip Flop

Present state	Input	Next state
Q	D	Q (t +l)
0	0	0
0	1	1
1	0	0
1	1	1

D Flip Flop

Procedure :

1. Make connections as shown in figure for each flip-flop one by one. (Refer pin diagram of ICs)
2. Connect +5 V to pin no. 14 and ground to pin no. 7 of ICs.
3. Connect pulsar switch output (Y) to clock input CP of flip-flop
4. Connect input I or 0 to inputs of flip-flops as per Truth Table shown.
5. Switch ON the instrument.
6. Press pulsar switch to get output.
7. Observe outputs on 10 bits LED display or logic probe.
8. Repeat above steps 4, 5, 6 for other input combinations.
9. Verify Truth Tables.

Observations :

1. Indeterminate state of RS flip-flop is determined in JK flip-flop.
2. Toggle state in JK flip-flop is eliminated in master slave flip-flop.

EXPERIMENT 8

Objective : Study of Crystal Oscillator

Components Needed:

S.N	Components	Quantity
1.	Resistance 330R	3
2.	Crystal 1 MHz	1
3.	Capacitor 0.01 μ FD 100 PF	1 1
4.	IC 7404 Hex Inverter	1

Logic diagram

 


Figure 10

Procedure :

1. Make connections as shown in figure (Refer pin diagram of ICs)
2. Connect +5V to pin no. 14 and connect ground to pin no. 7 of IC 7404.
3. Switch ON the instrument.
4. Observe oscillator output on oscilloscope.
5. Measure the frequency.
6. Compare with frequency of crystal.

Observation and Result:

Crystal oscillator frequency depends solely on crystal dimensions and independent of any other parameter.

EXPERIMENT 9

Objective: Study of 4 bit Binary up down Counter

Components Needed:

S.N	Components	Quantity
1.	IC 74107 Dual JK flip flop with clear	2
2.	IC 7408 2 input AND Gate	2
3.	IC 7432 2 input OR Gate.	1

Logic diagram:

 


Figure 11

Procedure :

- 1.** Make connection as shown in figure (Refer pin diagram of ICs)
- 2.** Connect +5V to pin no.14 and ground to pin no. 7 of ICs.
- 3.** Connect +5V to the UP terminal of Counter and ground to DOWN terminal.
- 4.** Connect ground to clear input of flip flop.
- 5.** Disconnect ground from clear input of flip flop.
- 6.** Connect Y output of pulsar switch to clock input of flip-flop.
- 7.** Switch ON the instrument.
- 8.** Press pulsar switch.
- 9.** Observe outputs on 10 bits LED display.
- 10.** Press pulsar switch 12 times and observe change in output. It will follow Sequence as shown in Truth Table for UP counter.
- 11.** Connect + 5V to DOWN terminal and ground to UP terminal.
- 12.** Repeat steps 6, 7, and 10 for counter to count down.
- 13.** Verify Truth Table.

Truth Table:

Up Counter

A4	A3	A2	A1
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
1	0	1	0
1	0	1	1
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1

Down Counter

A4	A3	A2	A1
1	1	1	1
1	1	1	0
1	1	0	1
1	1	0	0
1	0	1	1
1	0	1	0
1	0	0	1
1	0	0	0
0	1	1	1
0	1	1	0
0	1	0	1
0	1	0	0
0	0	1	1
0	0	1	0
0	0	0	1
0	0	0	0

EXPERIMENT 10

Objective: Study of Johnson Counter

Components Needed:

S.N	Components	Quantity
1.	IC 7474 D flip flop	2
2.	IC 7408 2 input AND Gate	2

Logic diagram:

 


Figure 12

Truth Table :

Sr. No.	Flip flop output A	B	C	E	AND Gate required for output
1	0	0	0	0	A'E'
2	1	0	0	0	AB'
3	1	1	0	0	BC'
4	1	1	1	0	CE'
5	1	1	1	1	AE
6	0	1	1	1	A'B
7	0	0	1	1	B'C
10	0	0	0	1	C'E

Procedure:

1. Make connections as shown in figure (Refer to pin diagram of ICs)
2. Connect +5 V to pin no. 14 and ground to pin no. 7 of ICs.
3. Connect ground to clear input of flip flop and disconnect it.
4. Connect A output of pulsar switch to clock input of flip-flops.
5. Switch ON the instrument.
6. Press pulsar switch.
7. Observe outputs on 10 bits LED display.
8. Press pulsar switch 7 times and observe change in output. It will follow Sequence as shown in Truth Table.
9. Verify Truth Table.
10. AND & NOT Gates can be used to make product terms of last column and can be observed on 10 bits LED display to know when a particular Combination occurs.

Result :

Johnson counter gives $2k$ distinguishable states with k flip-flop.

A large, light gray watermark of the sci-tech logo is centered on the page. It features a stylized 's' and 't' in a blue and green gradient, followed by the text 'sci-tech' in a bold, black, sans-serif font.

EXPERIMENT 11

Objective : Study of 4 Bit Serial in Parallel out Shift Register

Components Needed:

S.N	Components	Quantity
1.	IC 7474 D flip flop	1

Logic diagram :

 


Figure 13

Truth Table :

A	B	C	D
0	0	0	0
1	0	0	0
1	1	0	0
1	1	1	0
1	1	1	1

Procedure :

1. Make connections as shown in figure (Refer to pin diagram of ICs)
2. Connect +5V to pin no. 14 and ground to pin no. 7 of IC 7474.
3. Switch ON the instrument.
4. Clear all flip-flops by applying ground to clear input of flip-flops.
5. Apply +5V to serial input SI of shift register.
6. Connect A output of pulsar switches to clock input of flip-flops.
7. Trigger flip-flops four times by pressing pulsar switch 4 times.
8. Observe output of each flip-flop on 10 bits LED display. It will be as indicated in table.
9. As shown in table, 1 is shifted to right each time flip-flop is triggered.

EXPERIMENT 12

Objective: Study of 10 to 3 Line Encoder

Components Needed:

S.N	Components	Quantity
1.	IC 7432 2 input OR Gate	2

Logic diagram:

 


Figure 14

Truth Table:

D0	D1	D2	D3	D4	D5	D6	D7	x	y	z
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

Procedure:

(Use two 2 input OR Gate in place of one 4 input OR Gate.)

1. Make connections as shown in figure (Refer to pin diagram of ICs)
2. Connect +5 V to pin no. 14 and ground to pin no. 7 of IC 7432.
3. Connect input 1(+5V) or 0 (0V) to encoder circuit as shown in figure as per truth table.
4. Switch ON the instrument.
5. Observe outputs on 10 bits LED display.
6. Repeat step no. 3 and 5 for other input combination.
7. Verify Truth Table.

EXPERIMENT 13

Objective : Study of 3 to 10 Line Decoder

Components Needed:

S.N	Components	Quantity
1.	IC 7411 3 input AND Gate.	3
2.	IC 7404 Inverter.	1

Logic diagram :

 


Figure 12

Truth Table :

x	y	z	D0	D1	D2	D3	D4	D5	D6	D7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	1	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

Procedure :

1. Make connections as shown in figure (Refer to pin diagram of ICs)
2. Connect +5 V to pin no. 14 and ground to pin no. 7 of IC 7404 and IC 7411.
3. Connect input 1 or zero to decoder circuit as shown in figure as per Truth Table.
4. Switch ON the instrument.
5. Observe outputs on 10 bits LED display.
6. Repeat step no. 3 and 5 for other inputs.
7. Verify Truth Table.

A large, light gray watermark of the sci-tech logo and text is centered on the page.

EXPERIMENT 14

Objective : Study of Multiplexer and De-multiplexer Circuit

A. Multiplexer


Components Needed:

S.N	Components	Quantity
1.	IC 7411 3 input AND Gate.	2
2.	IC 7432 2 Input OR Gate.	1
3.	IC 7404 NOT Gate.	1

Logic diagram:

4 To 1 Line Multiplexer

Truth Table:

 

Selection line 1 (A)	Selection line 2 (B)	Input Selected (E)
0	0	I 1
0	1	I 2
1	0	I 3
1	1	I 4

Figure 16

Procedure:

1. Make connections as shown in figure (Refer pin diagram of ICs).
2. Connect + 5 V to pin no. 14 and ground to pin no.7 of ICs.
3. Apply inputs 1 or 0 to input lines 11, 12, 13, 14.
4. Connect 0 to selection lines S1 and S0 as shown in Truth Table.
5. Switch ON the power supply.
6. Observe outputs on 10 bits LED display or logic probe.
7. If input applied is square wave or pulse then CRO can be used to view Waveforms at output.
8. Repeat step 4 for other input combination.
9. Follow above steps and prove Truth Table.

B. De-multiplexer

Components Needed:

S.N	Components	Quantity
1.	IC 7404 NOT Gate	1
2.	IC 7410 NAND Gate	2

Logic diagram :

1 To 4 Line De-multiplexer :

 


Figure 17

Truth Table :

Input	Selection line	Selection line	Output Line	Output Line	Output Line	Output Line
E	S0	S1	D0	D1	D2	D3
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

Procedure :

1. Make connections as shown in figure (Refer pin diagram of ICs).
2. Connect + 5 V to pin no. 14 and ground to pin no.7 of ICs.
3. Apply inputs 1 or 0 to input E.
4. Connect 0 to selection lines S1 and S0 as shown in Truth Table.
5. Switch ON the instrument
6. Observe outputs on 10 bits LED display or logic probe.
7. If input applied is square wave or pulse then CRO can be used to view waveforms at output.
8. Repeat step 4 & 6 for other input combinations.
9. Follow above steps and prove Truth Table.

EXPERIMENT 15

Objective: Study of Pulse Stretcher Circuit

Components Needed:

S.N	Components	Quantity
1.	IC 7400 2 input NAND Gate	1
2.	Capacitors 0.01 MF	1
	0.022 MF	1
	0.033 MF	1
3.	Resistance 5600 Ω	2

Logic diagram:

 


Figure 110

Procedure:

1. Make connections as shown in figure (Refer pin diagram of ICs)
2. Select clock generator at 10 KHz & Connect Clock generator output to the terminal marked input.
3. Switch ON the Instrument.
4. Apply same pulse to ext trigger input of CRO for triggering time base.
5. See the output waveform on CRO.
6. Change value of capacitor C and observe the change in width.
7. Follow the above steps and complete table shown.

Observation :

Sr. No.	Capacitance	Pulse width at terminal 6
1	0 MF	
2	0.001 MF	
3	0.022 MF	
4	0.033 MF	

Result:

The width of output at point 3 is longer than that at A because it takes capacitor C time to charges up to the threshold voltage of Gate 2.

EXPERIMENT 16

Objective:

Study of method of Interfacing CMOS Logic family with TTL Logic family

Introduction:

The CMOS logic family can be operated at the same power supply voltage as TTL but with a sacrifice in speed. To operate the CMOS family at its maximum speed requires operation with V_{dd} equal to 12V. To interface with TTL requires a level shifting device. CMOS logic elements can easily drive other CMOS elements because of their high input resistance. However, most CMOS logic elements cannot provide the current required by a single load of the medium-power TTL series. To satisfy this current requirement requires high current CMOS buffer element.

Equipments Needed:

Component	Quantity
1. IC 7406 NOT Gate	1
2. IC 4001 NOR Gate	1
3. IC 4050 CMOS Buffer	1

Logic diagram:

 


Figure 19

Procedure:


1. Make connections as shown in figure (Refer pin diagram of ICs)
2. Connect +5 V to pin no. 14 and ground to pin no. 7 of IC 7406.
3. Connect + 12 V to pin no. 14 and ground to pin no. 7 of IC 4001.
4. Connect +5 V to pin no. 1 and ground to pin no. 10 of IC 4050.
5. View and sketch the waveform at
 - a. 4001 pin 1
 - b. 4001 pin 3
 - c. 4050 pin 2
 - d. 7406 pin 4

Result:


CMOS to TTL interface circuit is studied.

PIN DIAGRAMS OF ICS

 
54/7400
54H/74H00
54S/74S00
54LS/74LS00
QUAD 2-INPUT NAND GATE



 
54/7402
54S/74S02
54LS/74LS02
QUAD 2-INPUT NOR GATE



 54/7404
54H/74H04
54S/74S04
54S/74S04
54LS/74LS04
HEX INVERTER




 54/7406
HEX INVERTER BUFFER/ DRIVER
(WITH OPEN-COLLECTOR
A HIGH- VOLTAGE OUTPUT)




54/7408

 **54H/74H08
54S/74S08
54LS/74LS08
QUAD 2-INPUT AND GATE**




54/7411

 
**54H/74H11
54S/74S11
54LS/74LS11
TRIPLE 3-INPUT AND GATE**



 **4/7432
4S/74S32
4LS/74LS32
AD 2-INPUT OR GATE**




 **54/7474
54H/74H74
54S/74S74
54LS/74LS74
DUAL D-TYPE POSITIVE
EDGE TRIGGERED FLIP FLOP**




54/74107

 54LS/74LS107
DUAL JK FLIP FLOP
(WITH SEPARATE
CLEAR AND CLOCKS)



54LS/74LS86

QUAL 2-INPUT EXCLUSIVE OR GATE

 

sci-tech

A large, faded version of the sci-tech logo watermark, consisting of a green and purple swoosh followed by the text 'sci-tech' in a large, bold, sans-serif font.

SCI-TECH UK LIMITED

(Registration No: 1293368) (ISO 9001:2015 Certified, No: QMS/024098/0921)

Kemp House, 160 City Road, London EC1V 2NX,
UNITED KINGDOM

Tel: ++ 44 2081238067.

Website: www.scitechdidactic.com

E-mail: internationalsales@scitechdidactic.com;

nitinbarve@scitechdidactic.com; scitechenggprivateltd@yahoo.com
